

$$1a) \quad R = \frac{1}{\sigma} \cdot \frac{l}{A} (1 + \alpha \cdot \Delta T)$$

$$R_0 = \frac{1}{\sigma} \cdot \frac{l}{A} = \frac{1}{57 \cdot 10^6 \frac{S}{m}} \cdot \frac{20 \cdot 10^3 m}{\pi \cdot \left(\frac{10 \cdot 10^{-3}}{2}\right)^2 m^2} = 4,467 \Omega$$

$$\begin{aligned} \text{Winter } -20^\circ\text{C} \quad ; \quad R &= R_0 \cdot (1 + \alpha \cdot (T - T_0)) \\ &= 4,467 \Omega \cdot \left(1 + 0,004 \frac{1}{^\circ\text{C}} \cdot (-20^\circ\text{C} - 20^\circ\text{C})\right) \\ &= \underline{\underline{3,752 \Omega}} \end{aligned}$$

Normal/
Bezugstemperatur 20°C

$$R = R_0 = \underline{\underline{4,467 \Omega}}$$

Sommer $+40^\circ\text{C}$

$$R = \underline{\underline{4,825 \Omega}}$$

1 Punkt pro
wichtigem Wert
 $\Sigma 3 \text{ Pkt}$

b) $I = 40 \text{ A}$ Spannungsfall?

$$\Delta U = R \cdot I$$

$$\text{Winter } -20^\circ\text{C} \quad ; \quad \Delta U = 3,752 \Omega \cdot 40 \text{ A} = \underline{\underline{150 \text{ V}}}$$

Normal

$$\Delta U =$$

$$\underline{\underline{179 \text{ V}}}$$

$\Sigma 3 \text{ Pkt}$

Sommer

$$\Delta U =$$

$$\underline{\underline{193 \text{ V}}}$$

c) Verlustleistungen $P = \Delta U \cdot I = R \cdot I^2$

Winter

$$P_V = \underline{\underline{6 \text{ kW}}}$$

Normal

$$P_V = \underline{\underline{7,154 \text{ kW}}}$$

$\Sigma 3 \text{ Pkt}$

Sommer

$$P_V = \underline{\underline{7,72 \text{ kW}}}$$



d) Im Sommer $7,72 \text{ kW}$ mehr @ 24 h

$$W = 7,72 \text{ kW} \cdot 24 \text{ h} = 185,28 \text{ kWh} = \underline{\underline{185 \text{ MWh}}}$$

(2 Punkte)

2 Ersatzspannungsquelle

Linke Seite

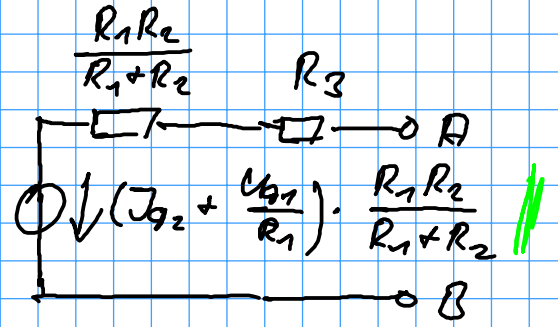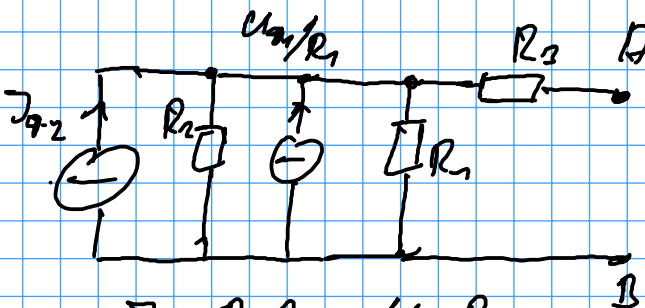


$$U_{UCC} = \frac{J_{g2} R_1 R_2 + U_{q1} R_2}{R_1 + R_2} \quad (1)$$

$$R_L = \frac{R_1 R_2}{R_1 + R_2} + R_3 = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1 + R_2} \quad (1)$$

$$J_{Koz} = \frac{U_{UCC}}{R_L} = \frac{J_{g2} R_1 R_2 + U_{q1} R_2}{R_1 R_2 + R_1 R_3 + R_2 R_3} \quad (1)$$


Rechts:

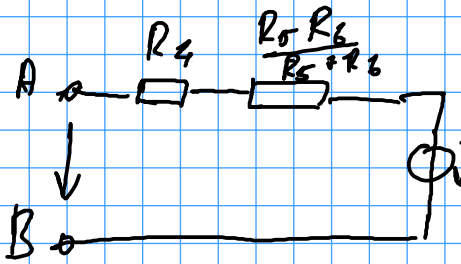

$$U_{UCC} = U_{q2} \quad (1)$$

$$R_R = R_4 + \frac{R_5 R_6}{R_5 + R_6} = \frac{R_4 R_5 + R_4 R_6 + R_5 R_6}{R_5 + R_6} \quad (1)$$
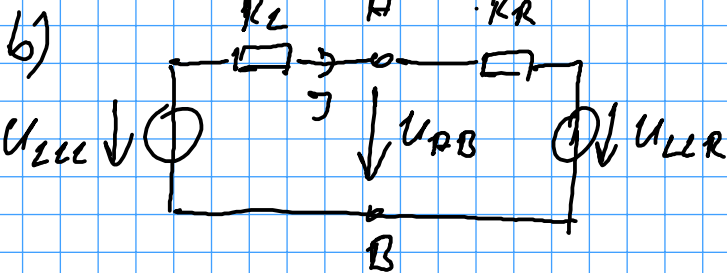
$$J_{KSR} = \frac{U_{UCC}}{R_R} = \frac{U_{q2} (R_5 + R_6)}{R_4 R_5 + R_4 R_6 + R_5 R_6} \quad (1)$$



Messungssatz:

$$J \cdot R_L + J \cdot R_R + U_{UCC} - U_{UCC} = 0$$


$$\Rightarrow J = \frac{U_{UCC} - U_{UCC}}{R_L + R_R} \quad (2)$$

$$U_{UB} = U_{UCC} - R_L \cdot J = U_{UCC} - R_L \cdot \frac{U_{UCC} - U_{UCC}}{R_L + R_R} = \frac{U_{UCC} \cdot R_L + U_{UCC} \cdot R_R}{R_L + R_R} \quad (2)$$

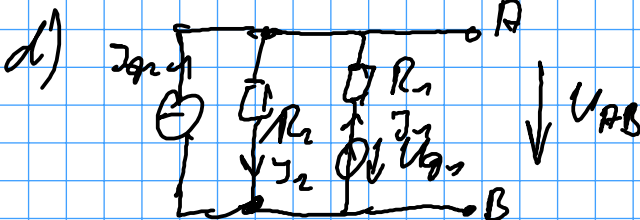c) Strom durch R_3 ist Null

\Rightarrow Kein Strom durch R_3, R_4, R_5, R_6 (1)

$$J_3 = J_4 = 0 \quad U_{UCC} = U_{UCC} = U_{q2} = \frac{J_{g2} R_1 R_2 + U_{q1} R_2}{R_1 + R_2} \quad (1)$$



(3 Pkt)

e) Now U_{q1} eingeschaltet

$$J_{21} = J_{11} = \frac{U_{q1}}{R_1 + R_2}$$

$$J_{12} = -J_{q2} = \frac{R_2}{R_1 + R_2}$$

$$J_{22} = J_{q2} = \frac{R_1}{R_1 + R_2}$$


$$J_1 = J_{11} + J_{12} = \frac{U_{q1} - J_{q2} R_2}{R_1 + R_2} \quad (1)$$

$$J_2 = J_{21} + J_{22} = \frac{U_{q1} + J_{q2} R_1}{R_1 + R_2} \quad (2)$$

$$P_{R1} = R_1 \cdot J_1^2 = R_1 \cdot \left(\frac{U_{q1} - J_{q2} R_2}{R_1 + R_2} \right)^2 \quad (3)$$

$$P_{R2} = R_2 \cdot J_2^2 = R_2 \cdot \left(\frac{U_{q1} + J_{q2} R_1}{R_1 + R_2} \right)^2 \quad (4)$$
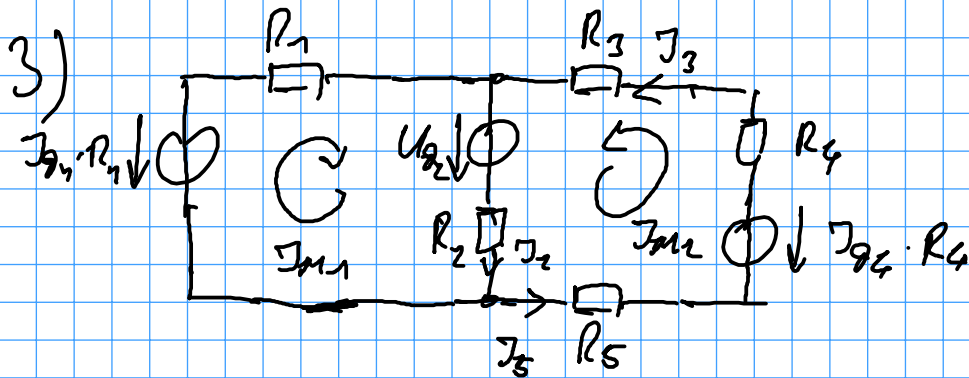
$$P_{ges} = P_{R1} + P_{R2} = R_1 \left(\frac{U_{q1} - J_{q2} R_2}{R_1 + R_2} \right)^2 + R_2 \left(\frac{U_{q1} + J_{q2} R_1}{R_1 + R_2} \right)^2 \quad (5)$$



GLS

$$\begin{pmatrix} R_1 + R_2 & R_2 \\ R_2 & R_2 + R_3 + R_4 + R_5 \end{pmatrix} \begin{pmatrix} J_{M1} \\ J_{M2} \end{pmatrix} = \begin{pmatrix} J_{g1} R_1 - U_{g2} \\ J_{g2} R_4 - U_{g2} \end{pmatrix} \quad 5 \text{ Pkt}$$

b) Cramer'sche Regel

$$J_{M1} = \frac{(J_{g1} R_1 - U_{g2})(R_2 + R_3 + R_4 + R_5) - (J_{g2} R_4 - U_{g2}) R_2}{(R_1 + R_2)(R_2 + R_3 + R_4 + R_5) - R_2^2} \quad (2)$$

$$J_{M2} = \frac{(J_{g2} R_4 - U_{g2})(R_1 + R_2) - (J_{g1} R_1 - U_{g2}) R_2}{(R_1 + R_2)(R_2 + R_3 + R_4 + R_5) - R_2^2} \quad (2)$$



c) Zweigströme

$$\begin{aligned} R_1: J_1 &= J_{g1} - J_{M1} \\ R_2: J_2 &= J_{M1} + J_{M2} \\ R_3: J_3 &= J_{M2} \\ R_4: J_4 &= J_{g2} - J_{M2} \\ R_5: J_5 &= J_{M2} \end{aligned} \quad (5)$$

d)

$$\begin{pmatrix} 10 & 10 \\ 10 & 1012 \end{pmatrix} \begin{pmatrix} J_{M1} \\ J_{M2} \end{pmatrix} = \begin{pmatrix} 0 \\ 10 \end{pmatrix} \text{ A}$$
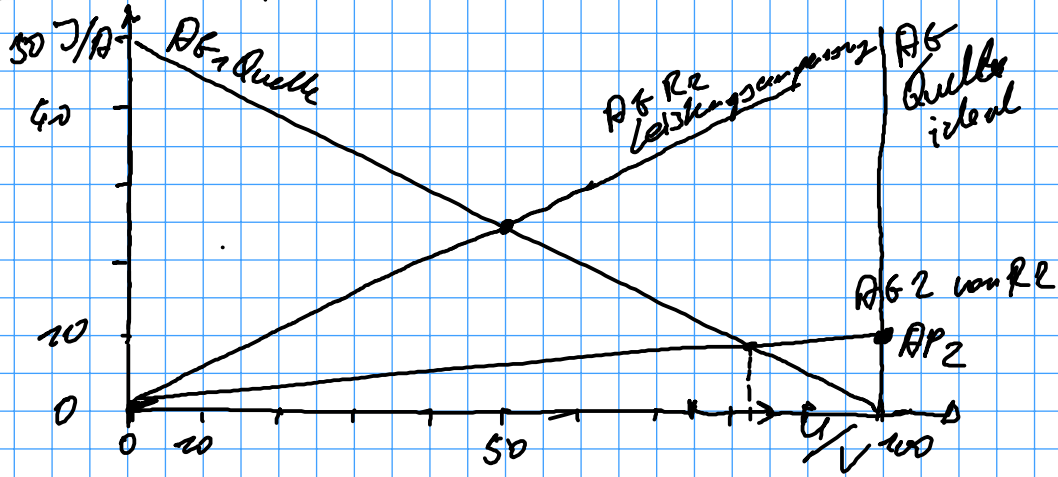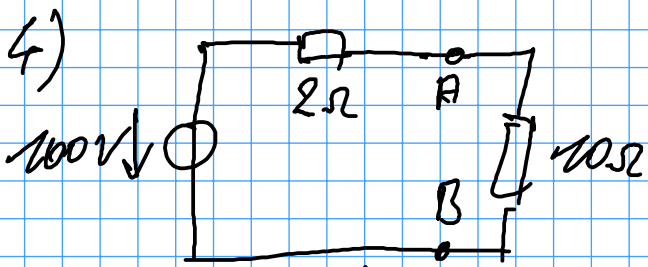
$$\begin{aligned} J_{M1} &= -97,8 \mu\text{A} ; J_{M2} = 9,88 \mu\text{A} \\ J_1 &= 1,0098 \text{ mA} ; J_2 = 9,928 \text{ mA} \\ J_3 &= 1,012 \text{ mA} ; J_4 = J_5 = 9,88 \mu\text{A} \end{aligned} \quad (5)$$



b) AP1: $U = 83,3 \text{ V}$; $I = 8,33 \text{ A}$ (2)

c) AP2: $U = 100 \text{ V}$; $I = 10 \text{ A}$ (2)

d) Leistungsanpassung $U_{R_1} = U_{R_2} = \frac{1}{2} U_0$

AP: $U = 50 \text{ V}$; $I = 25 \text{ A}$; $R_1 = R_2 = 2 \Omega$ (3)

e) Wirkungsgrade

1) $\eta = \frac{I^2 \cdot R_2}{I^2 \cdot (R_1 + R_2)} = \frac{10}{12} = 83,3\%$

2) $\eta = 100\%$

3) $\eta = 50\%$

(3)