
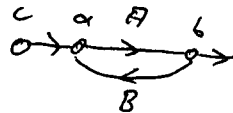


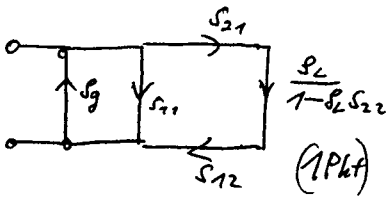(a) Berechnen Sie  $\frac{b}{a}$ , die Transmission




$$a \cdot A = b$$

$$c + b \cdot B = a$$

$$\Leftrightarrow (c + b \cdot B) \cdot A = b$$

$$\Leftrightarrow c \cdot A + b \cdot B \cdot A = b$$
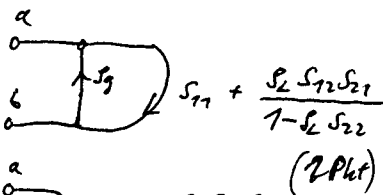
$$\Leftrightarrow b = c \cdot \frac{A}{1 - BA}$$



$$\frac{S_{11} + \frac{S_L S_{12} S_{21}}{1 - S_L S_{22}}}{1 - S_g \cdot \left( S_{11} + \frac{S_L S_{12} S_{21}}{1 - S_L S_{22}} \right)}$$

$$= \frac{S_{11} (1 - S_L S_{22}) + S_L S_{12} S_{21}}{1 - S_L S_{22} - S_g S_{11} (1 - S_L S_{22}) + S_L S_g S_{12} S_{21}} \quad (1 \text{ Pkt})$$

(b) Unter der Voraussetzung, dass  $S_g$  ideal  $= 0$  ist, bestimmen Sie  $S_L$  abhängig von  $\alpha$ ! (Wenn Sie Ihre Lösung aus (a) nicht erhalten, dann rechnen Sie (a) nochmals ohne  $S_g$ )

$$\frac{b}{a} = S_{11} + \frac{S_L S_{12} S_{21}}{1 - S_L S_{22}}$$

$$\Leftrightarrow \left( \frac{b}{a} - S_{11} \right) \cdot (1 - S_L S_{22}) = S_L S_{12} S_{21}$$

$$\Leftrightarrow \frac{b}{a} - S_{11} - S_L S_{22} \left( \frac{b}{a} - S_{11} \right) = S_L S_{12} S_{21}$$

$$\Rightarrow \frac{b}{a} S_{11} = S_L \left[ S_{12} S_{21} + S_{22} \left( \frac{b}{a} - S_{11} \right) \right]$$

$$\Rightarrow S_L = \frac{\cancel{\frac{S_{12} S_{22}}{a - S_{11}}} + S_{22} \frac{b}{a} - S_{11}}{\cancel{\frac{S_{12} S_{21}}{b - S_{11}}} + S_{22} \frac{b}{a} - S_{11}}$$

insgesamt  
(2 Pkt)

(c) Bestimmen Sie die Koeffizienten  $A, B, C, D$  in der Formel

$$S_L = \frac{A \frac{b}{a} + B}{C \frac{b}{a} + D}$$

$$\Rightarrow A=1; B=-S_{11}; C=S_{22}; D=S_{12} S_{21} - S_{22} S_{11}$$

1 Pkt

~~(d) Unter der Annahme, dass es sich bei dem zweidimensionalen  $\vec{E}$ - $\vec{H}$ -Feld um eine einfache, sehr gut an beiden Seiten angepasste Leitung handelt, kann man  $S_{11} = S_{22} = 0, 1$  und  $S_{12} = S_{21} = \sqrt{1 - S_{11}^2} = 0,995$  annehmen. Geben Sie mit diesen Werten  $S_L$  an~~

~~$$S_L = \frac{\frac{a}{b} - 0,1}{0,16 - 0,8701}$$~~


(d) Für  $S_{11} = S_{22} = 0$  und  $S_{12} = S_{21} = 0$  (ideale Leitung ohne Phasen drehung) gehen Sie zu (c) zurück und berechnen Sie mit  $S_0 \neq 0$  erneut  $S_L$

$$\frac{b}{a} = \frac{S_L}{1 - S_L S_0} \quad (1 \text{ Punkt})$$



$$\frac{b}{a} - S_L S_0 \frac{b}{a} = S_L$$

$$\Rightarrow S_L = \frac{b/a}{1 + S_0 b/a}$$

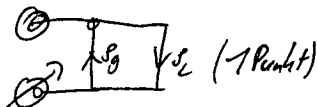Zeichnen Sie zuerst den vereinfachten Schaltplan




# 5) Signalflussgraf

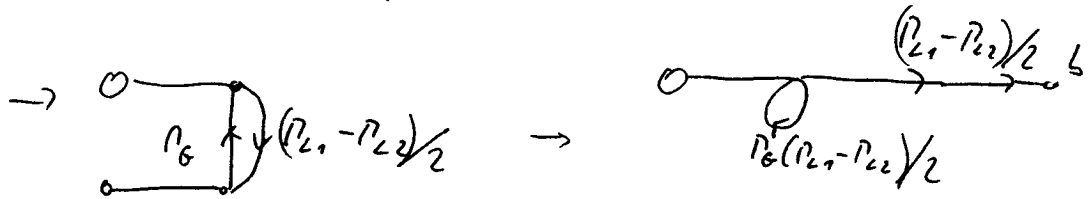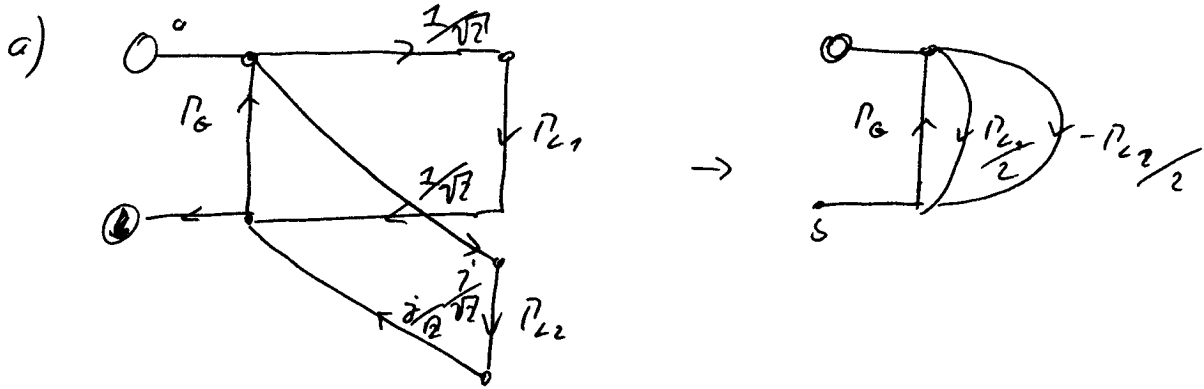

$$\frac{b}{a} = \frac{P_{L1} - P_{L2}}{1 - P_G(P_{L1} - P_{L2})/2} \cdot \frac{1}{2} \quad (7)$$

b) Analog jedoch dann  $\frac{b}{a} = \frac{(P_{L1} + P_{L2})}{1 - P_G(P_{L1} + P_{L2})/2} \cdot \frac{1}{2} \quad (7)$



c) Allgemein:

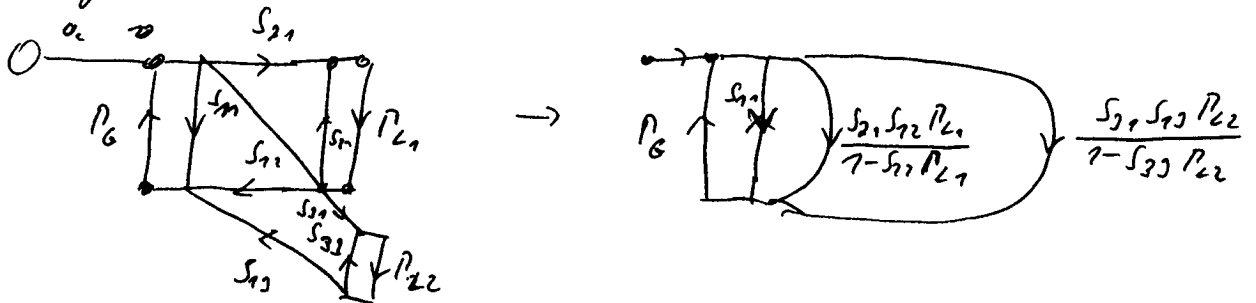

$$\frac{b}{a} = \frac{A}{1 - AP_G} = \frac{S_{21} + \frac{S_{21} S_{22} P_{L1}}{1 - S_{22} P_{L1}} + \frac{S_{31} S_{32} P_{L2}}{1 - S_{32} P_{L2}}}{1 - \left( \frac{S_{21} (1 - S_{22} P_{L1}) (1 - S_{32} P_{L2}) + S_{21} S_{22} P_{L1} + S_{31} S_{32} P_{L2}}{(1 - S_{22} P_{L1}) (1 - S_{32} P_{L2}) - S_{21} (1 - S_{22} P_{L1}) (1 - S_{32} P_{L2}) - S_{21} S_{22} P_{L1} - S_{31} S_{32} P_{L2}} \right) P_G} \quad (3)$$



d) Variante a, da hier nur die Differenz der Reflexionen der beiden Stufen auftritt, die geringer ist als die Summe, wenn die beiden Vierpolstufen weitergehend überblickbar sind.

e)

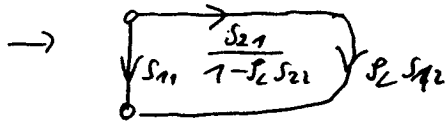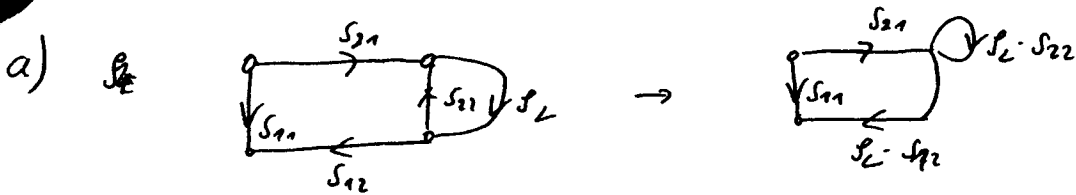

$$\rightarrow \underline{\underline{S_E = S_{11} + \frac{P_L \cdot S_{12} \cdot S_{21}}{1 - P_L \cdot S_{22}}}}$$

(1)

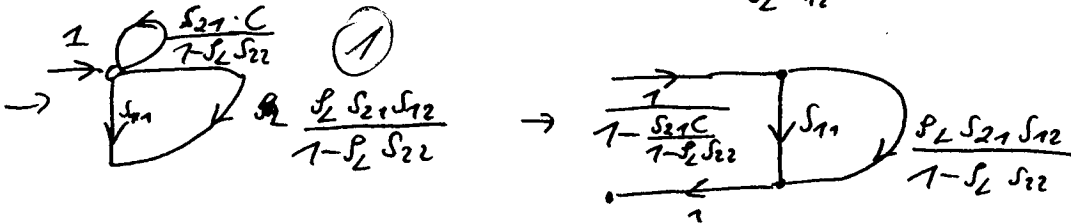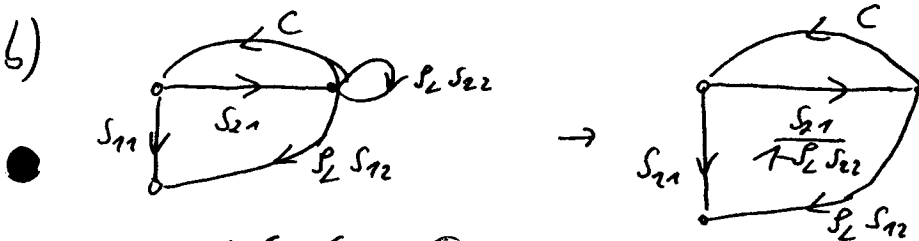

$$S_E = \frac{1}{1 - \frac{S_{21}C}{1 - P_L S_{22}}} \cdot \left( S_{11} + \frac{P_L S_{21} S_{12}}{1 - P_L S_{22}} \right)$$

$$= \frac{S_{11} - P_L S_{11} S_{22} + P_L S_{21} S_{12}}{1 - P_L S_{22} - S_{21} C}$$

(2)

c) Es muss  $P_L S_{22} = -S_{21} C \Leftrightarrow \underline{\underline{C = -\frac{P_L S_{22}}{S_{21}}}}$

(1)

da  $|P_L| < 1$ ;  $|S_{22}| < 1$  und  $|S_{21}| > 1$  gilt (in der Regel) folgt dann auch  $|C| < 1$ , womit C mit passiven EGmen zu realisieren ist

(1)

(2)

d) Abgelesen:


$$b_E = K \cdot \alpha_A + K^2 P_A \alpha_S + K^3 P_E P_S P_A \cdot b_E$$

$$\Leftrightarrow \underline{\underline{b_E = \frac{K \alpha_A + K^2 P_A \alpha_S}{1 - K^3 P_E P_S P_A}}}$$

(2)

e) Mit  $P_A = 0$  sind wir diese Koppelprobleme & auch noch das Schleifenproblem los!

(1)

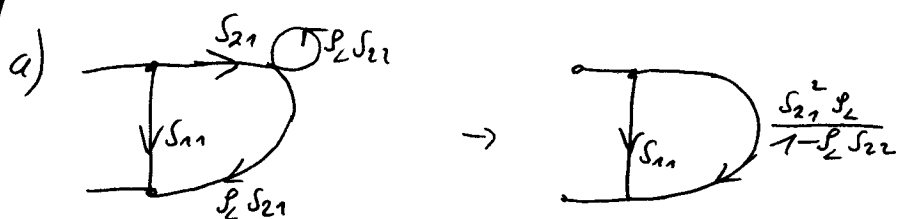

$$\frac{b}{a} = S_{11} + \frac{S_{21}^2 p_L}{1 - p_L S_{22}}$$

$$b) \frac{b}{a} (1 - p_L S_{22}) = S_{11} + S_{21}^2 p_L - p_L \cdot S_{11} S_{22}$$

$$\Leftrightarrow \frac{b}{a} - S_{11} = p_L \cdot (S_{21}^2 + \frac{b}{a} S_{22}) - S_{11} S_{22}$$

$$\Leftrightarrow p_L = \frac{\frac{b}{a} - S_{11}}{S_{21}^2 + \frac{b}{a} S_{22} - S_{11} S_{22}} = \frac{0,5 - 0,2}{0,64 + 0,5 \cdot 0,2 - 0,04} = \frac{0,3}{0,7} = \underline{\underline{\frac{3}{7}}}$$

c)  $p_L = 0$ :  $0,1 = S_{11}$  (1)

$p_L = -1$ :  $-\frac{7}{11} = S_{11} + \frac{S_{21}^2}{1 + S_{22}}$  (2)

$p_L = 1$ :  $1 = S_{11} + \frac{S_{21}^2}{1 - S_{22}}$  (3)

d)  $S_{11} = 0,1$

e) aus  $p_L = 1$ :  $1 = S_{11} + S_{21}^2$

$\Leftrightarrow S_{21}^2 = 0,9$ ;  $S_{22} = 0,9487$


f) (2):  $\frac{7}{11} \cdot (1 + S_{22}) - S_{11} = -S_{21}^2 = (\frac{7}{11} - S_{11}) \cdot (1 + S_{22})$

(3):  $(1 - S_{22}) - S_{11} = S_{21}^2 = (1 - S_{11}) \cdot (1 - S_{22})$



Summe der Gleichungen:  $0 = -\frac{7}{11} - S_{11} + 1 - S_{11} + S_{22} \cdot (\frac{7}{11} - S_{11} - 1 + S_{11})$

$\Leftrightarrow \frac{2S_{11} - \frac{18}{11}}{-\frac{18}{11}} = \frac{22S_{11} - 18}{-18} = S_{22} = \underline{\underline{0,1}}$

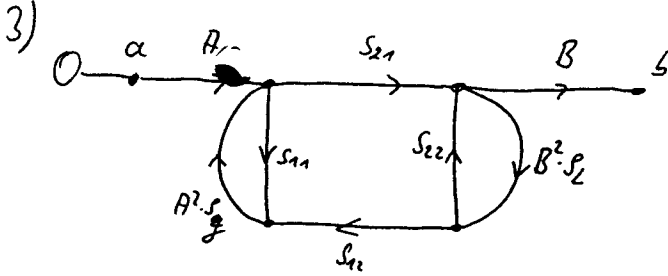$\Rightarrow S_{21}^2 = (1 - S_{11}) \cdot (1 - S_{22}) = 0,81 \Rightarrow \underline{\underline{S_{21} = 0,9}}$



mit  $S_L = 0$ :

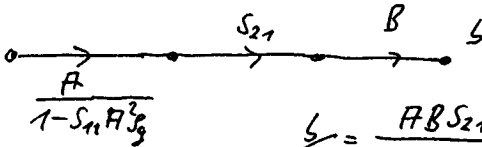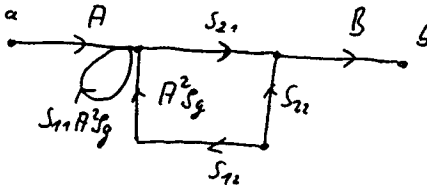


$$\frac{A}{1 - S_{11} A^2 S_g}$$


$$\frac{B}{\alpha} = \frac{A B S_{21}}{1 - S_{11} A^2 S_g}$$

(2)

b)  $S_L \neq 0$

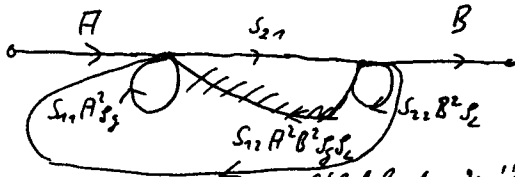

Schleife liegt außen!!

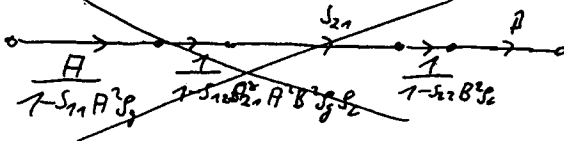

$$\frac{B}{\alpha} = \frac{A S_{21} B}{(1 - S_{11} A^2 S_g) (1 - S_{12} S_{21} A^2 B^2 S_g S_L) (1 - S_{22} B^2 S_L)}$$

$$\frac{B}{\alpha} = \frac{A S_{21} B}{(1 - S_{11} A^2 S_g) \cdot (1 - S_{22} B^2 S_L) - A^2 B^2 S_{12} S_g S_L}$$

(2)

$$3c) S_{21} = \frac{b/a \cdot (1 - S_{11} \Gamma^2 \Gamma_g)}{\Gamma B} \quad (1)$$

$$d) S_{21} = \frac{b}{a} \cdot (1 - S_{11} \Gamma_g)$$

$$S_{11} \text{ positiv: } S_{11} = -1 \dots 1$$

$$\Gamma_g = -10 \text{ dB} \approx 0,316 \Rightarrow S_{21} = \frac{b}{a} \cdot (0,684 \dots 1,316)$$

$$\Gamma_g = -20 \text{ dB} \approx 0,1 \Rightarrow \underline{\underline{S_{21} = \frac{b}{a} \cdot (0,9 \dots 1,1)}} \quad (2)$$