
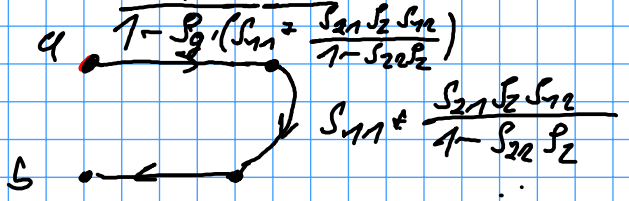
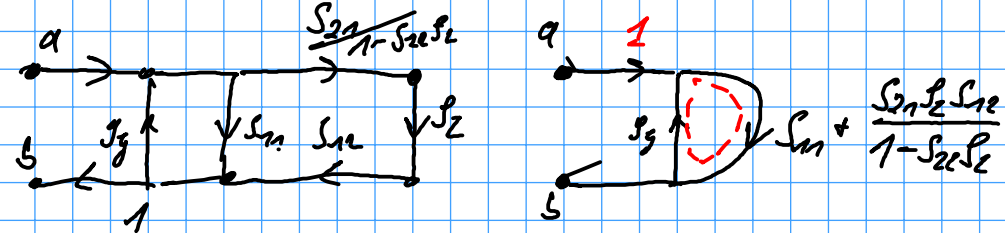


Signalflussgraphen

1a)

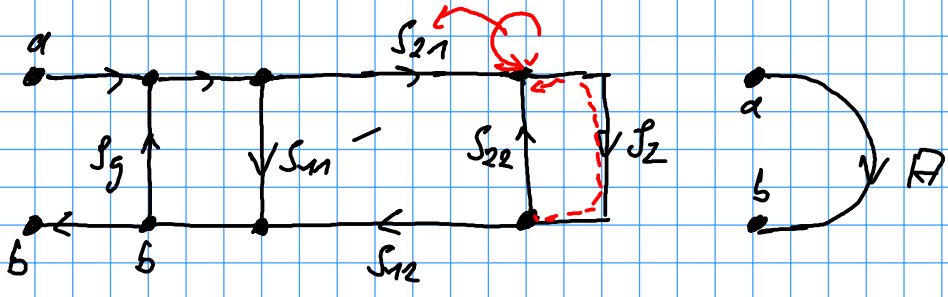

$$\frac{b}{a} = \frac{S_{11} + \frac{S_{21} S_{g2} S_{12}}{1 - S_{22} S_{g2}}}{1 - S_{g2} \left(S_{11} + \frac{S_{21} S_{g2} S_{12}}{1 - S_{22} S_{g2}} \right)}$$

$$= \frac{S_{11} (1 - S_{22} S_{g2}) + S_{21} S_{g2} S_{12}}{1 - S_{22} S_{g2} - S_{g2} S_{11} (1 - S_{22} S_{g2}) - S_{g2} S_{21} S_{g2} S_{12}}$$

b)
$$\frac{b}{a} = \frac{S_{21} S_{g2} S_{12}}{1 - S_{g2} S_{21} S_{g2} S_{12}}$$

$$\frac{b}{a} = S_{21} S_{g2} S_{12} + \frac{b}{a} \cdot S_{g2} S_{21} S_{g2} S_{12} \Rightarrow S_{g2} (S_{21} S_{12} + \frac{b}{a} S_{g2} S_{21} S_{12})$$

$$\Leftrightarrow S_{g2} = \frac{\frac{b}{a}}{S_{21} S_{12} \cdot (1 + \frac{b}{a} S_{g2})}$$

c)
$$S_{g2} = \frac{A \frac{b}{a} + B}{C \cdot \frac{b}{a} + D} \quad A=1, B=0$$

$$C = S_{21} S_{12} S_{g2}; D = S_{21} S_{12}$$

Wird zur Fehlerkorrektur bspw. bei relativen Netzwerkanalysatoren verwendet.

$$d) \frac{b}{a} = \frac{S_{11}(1 - S_{22}S_2) + S_{21}S_2S_{12}}{1 - S_{22}S_2 - S_2 S_{11}(1 - S_{22}S_2) - S_2 S_{21}S_2S_{12}}$$






mit $S_2 = 0$

$$\frac{b}{a} = \frac{S_{11} - S_{22}S_{11}S_2 + S_{21}S_2S_{12}}{1 - S_{22}S_2}$$

$$\Leftrightarrow \frac{b}{a} - S_{11} = S_2 \cdot (-S_{11}S_{22} + S_{21}S_{12} + S_{22}\frac{b}{a})$$


$$S_2 = \frac{\frac{b}{a} - S_{11}}{\frac{b}{a}S_{22} + S_{21}S_{12} - S_{11}S_{22}}$$

2)

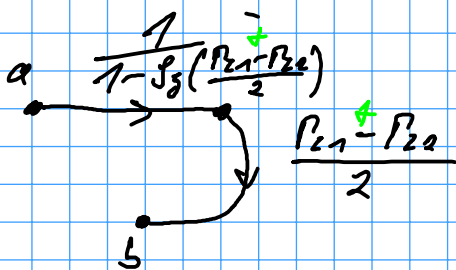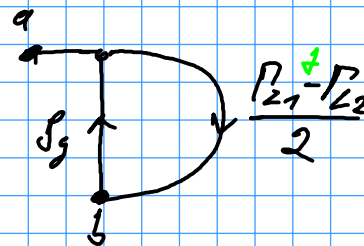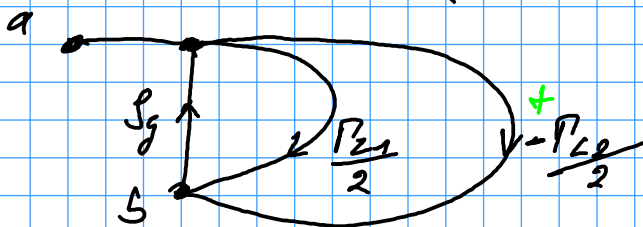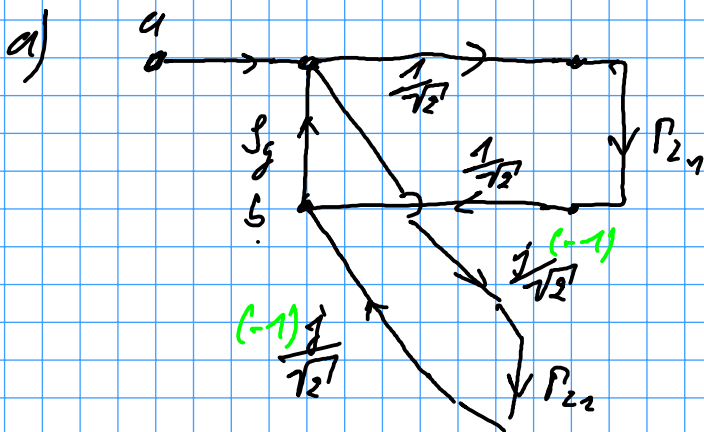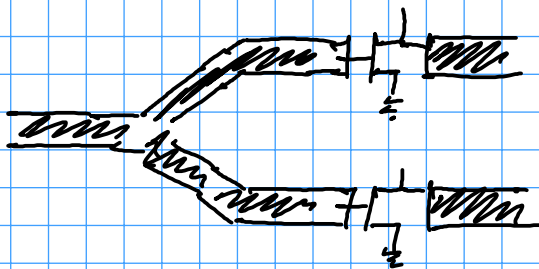

$$\frac{b}{a} = \frac{P_{21} + P_{22}}{2 - S_2(P_{21} + P_{22})}$$
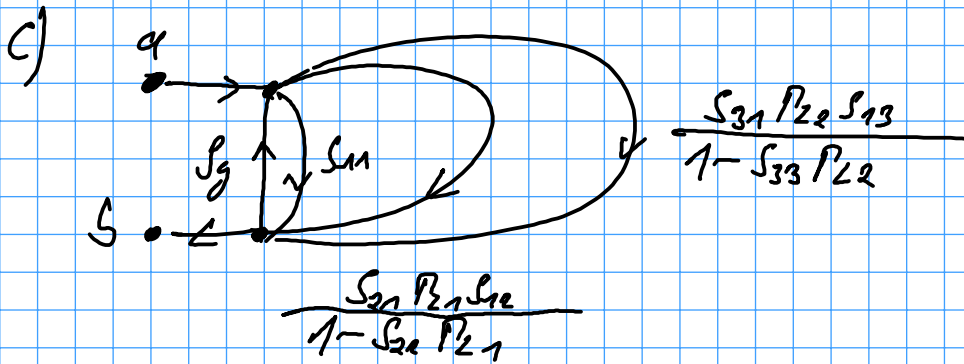
$$b) \frac{b}{a} = \frac{P_{21} + P_{22}}{2 - S_g (P_{21} + P_{22})}$$



$$S_{11} + \frac{S_{21} P_{21} S_{12}}{1 - S_{22} P_{21}} + \frac{S_{31} P_{22} S_{13}}{1 - S_{33} P_{22}}$$

$$= \frac{S_{11} (1 - S_{22} P_{21}) (1 - S_{33} P_{22}) + S_{21} S_{12} P_{21} (1 - S_{33} P_{22}) + S_{21} P_{22} S_{12} (1 - S_{22} P_{21})}{(1 - S_{22} P_{21}) (1 - S_{33} P_{22})} = A$$


$$\frac{b}{a} = \frac{A}{1 - S_g \cdot A} = \frac{S_{11} (1 - S_{22} P_{21}) (1 - S_{33} P_{22}) + S_{21} S_{12} P_{21} (1 - S_{33} P_{22}) + S_{21} P_{22} S_{12} (1 - S_{22} P_{21})}{(1 - S_{22} P_{21}) (1 - S_{33} P_{22}) - S_g [S_{11} (1 - S_{22} P_{21}) (1 - S_{33} P_{22}) + S_{21} S_{12} P_{21} (1 - S_{33} P_{22}) + S_{21} P_{22} S_{12} (1 - S_{22} P_{21})]}$$

d) Variante a ist zu korrigieren, weil die Reflexion $\frac{b}{a}$ minimal wird bei $P_{21} = P_{22}$ sogar verschwindet.


e) $P_{21} = 1$; Reflexionsfaktor für Amplituden
 $|P_{22}| = -10 \text{ dB}$ $P_{22} = \frac{1}{\sqrt{10}} \approx 0,316$
 $|P_G| = -20 \text{ dB}$ $P_G = \frac{1}{10} = 0,1 = S_g$

a) $\frac{b}{a} = \frac{P_{21} - P_{22}}{2 - S_g (P_{21} - P_{22})} = \frac{1 - 0,316}{2 - 0,1 \cdot (1 - 0,316)} = \underline{0,354} \hat{=} -9 \text{ dB}$

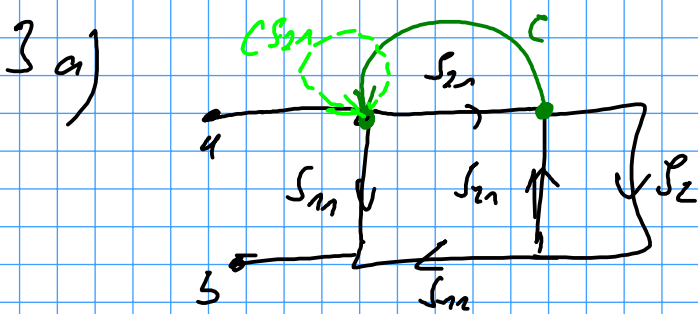b) $\frac{b}{a} = \frac{P_{21} + P_{22}}{2 - S_g (P_{21} + P_{22})} = \dots = \underline{0,709} \hat{=} -3 \text{ dB}$


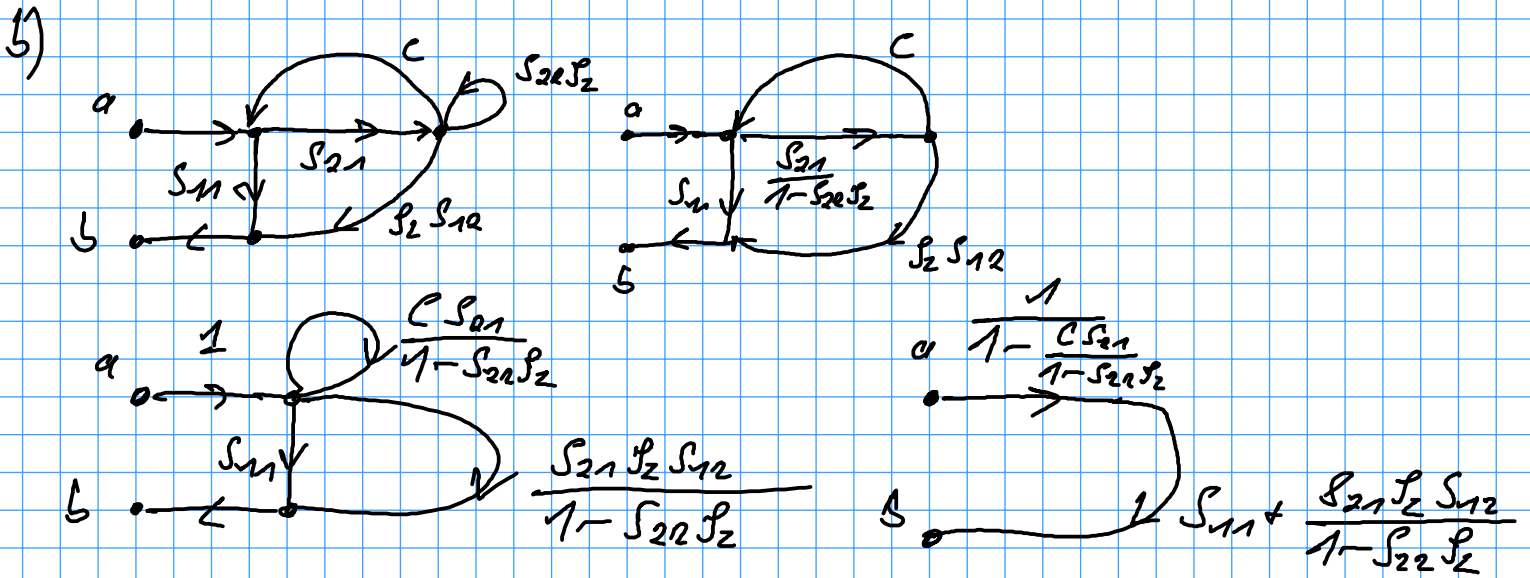
$$\frac{b}{a} = S_{11} + \frac{S_{21} S_2 S_{12}}{1 - S_{22} S_2}$$



$$\frac{b}{a} = \frac{S_{11}(1 - S_{22} S_2) + S_{21} S_2 S_{12}}{1 - S_{22} S_2 - C S_{21}}$$

das ist die Rückkopplung insgesamt.

c)


$$0 = -S_{22} S_2 - C S_{21} \quad \Leftrightarrow \quad C = \frac{-S_2 S_{22}}{S_{21}}$$

ist C passiv realisierbar?

$|S_{12}| < 1$, $|S_{22}| < 1$, $|S_{21}| > 1$ Verstärker / Transistor

$\Rightarrow |C| < 1$ also passiv realisierbar.

d)

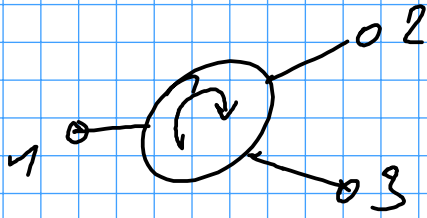

idealerweise Transmission von $1 \rightarrow 2$, aber nicht von $2 \rightarrow 1$ und $1 \rightarrow 3$
 $2 \rightarrow 3$; $3 \rightarrow 1$

S-Parameter

$$\begin{pmatrix} b_1 \\ b_2 \\ b_3 \end{pmatrix} = \begin{pmatrix} 0 & 0 & S_{13} \\ S_{23} & 0 & 0 \\ 0 & S_{32} & 0 \end{pmatrix} \begin{pmatrix} a_1 \\ a_2 \\ a_3 \end{pmatrix}$$

$$b_E = K \cdot a_R + K^2 \cdot \gamma_R \cdot a_S + K^3 \cdot \gamma_E \cdot \gamma_S \cdot \gamma_R \cdot b_E$$


$$b_E = \frac{K a_R + K^2 \gamma_R a_S}{1 - K^3 \gamma_E \gamma_R \gamma_S}$$

e)

γ_R muss optimal werden, wenn $\gamma_R = 0$ ist, sind Sender und Empfänger ideal entkoppelt.
 Die Koppelung entspricht $K^2 \cdot \gamma_R$.

f)

a)

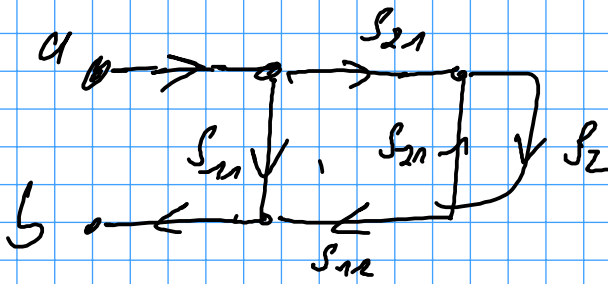

$$\frac{b}{a} = S_{11} + \frac{S_{21} S_2 S_{12}}{1 - S_{22} S_2}$$

$$b) \quad 0,5 = 0,2 + \frac{0,64 S_2}{1 - 0,2 S_2}$$

$$\Leftrightarrow 0,3 \cdot (1 - 0,2 S_2) = 0,64 S_2$$

$$\Leftrightarrow 0,3 = 0,7 \cdot s_2 \quad \Leftrightarrow \quad s_2 = \frac{3}{7} = \underline{\underline{0,429}}$$

$$c) \quad \frac{b}{a} = s_{11} + \frac{s_{21} s_{12} s_2}{1 - s_{22} s_2}$$

$$s_2 = 0 \quad \frac{b}{a} = s_{11} \quad \Rightarrow \quad 0,1 = s_{11}$$

$$s_2 = 1 \quad \frac{b}{a} = s_{11} + \frac{s_{21} s_{12}}{1 - s_{22}} \quad 1 = s_{11} + \frac{s_{21} s_{12}}{1 - s_{22}}$$

$$s_2 = -1 \quad \frac{b}{a} = s_{11} - \frac{s_{21} s_{12}}{1 + s_{22}} \quad -\frac{7}{11} = s_{11} - \frac{s_{21} s_{12}}{1 + s_{22}}$$

$$d) \quad s_{11} = 0,1$$

$$e) \quad s_{22} = 0 \quad \text{mit } s_2 = 1 \quad 1 = s_{11} + s_{12}^2$$

$$\Leftrightarrow s_{12} = \sqrt{1 - s_{11}} = \sqrt{0,9} = \underline{\underline{0,9487}}$$

$$f) \quad \begin{array}{l} 1 - s_{11} = \frac{s_{21}^2}{1 - s_{22}} \\ -\frac{7}{11} - s_{11} = \frac{-s_{21}^2}{1 + s_{22}} \end{array} \quad \text{v} \quad \frac{1 - s_{11}}{-\frac{7}{11} - s_{11}} = \frac{1 + s_{22}}{1 - s_{22}}$$







$$\Leftrightarrow A(1 - s_{22}) = -1 - s_{22}$$

$$\Leftrightarrow A + 1 = s_{22}(A - 1) \quad \Leftrightarrow \quad s_{22} = \frac{A + 1}{A - 1} = \underline{\underline{0,1}}$$

$$\rightarrow s_{21}^2 = (1 - s_{11})(1 - s_{22}) = 0,81$$

$$\underline{\underline{s_{21} = 0,9}}$$

5)

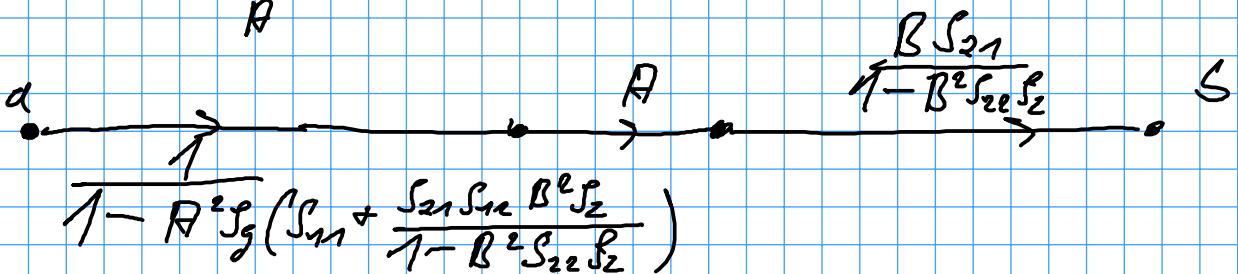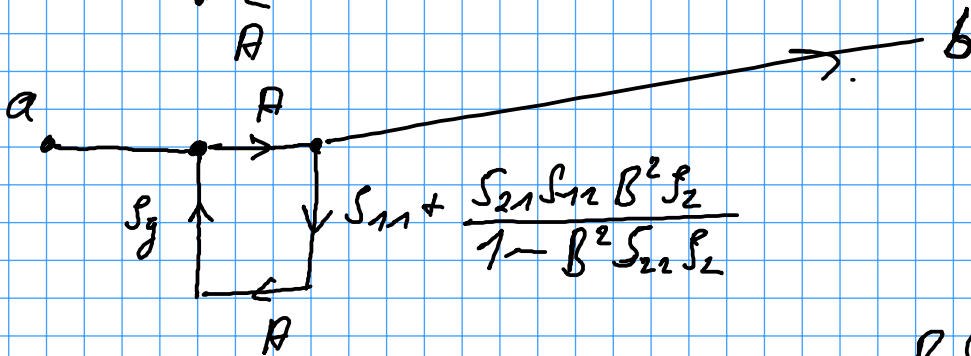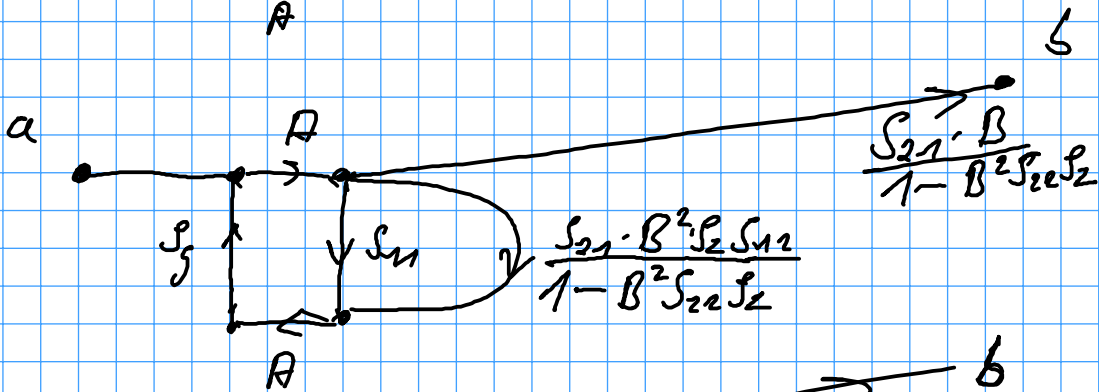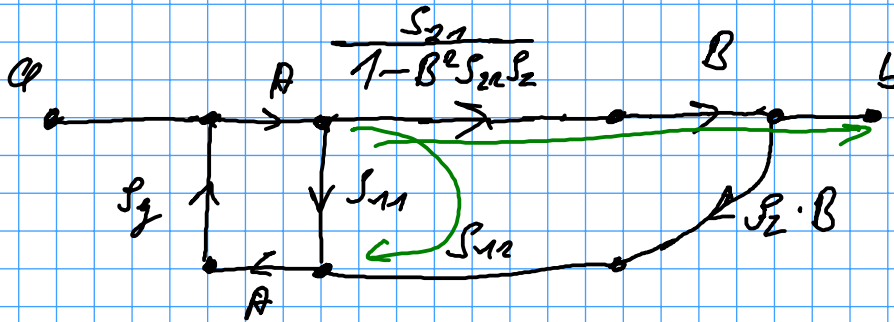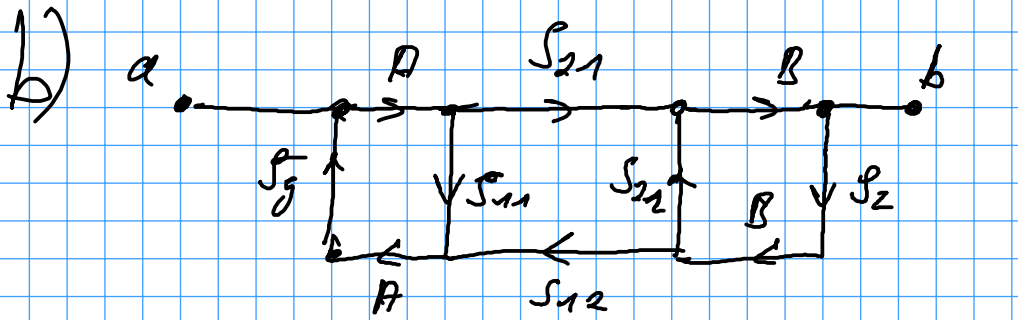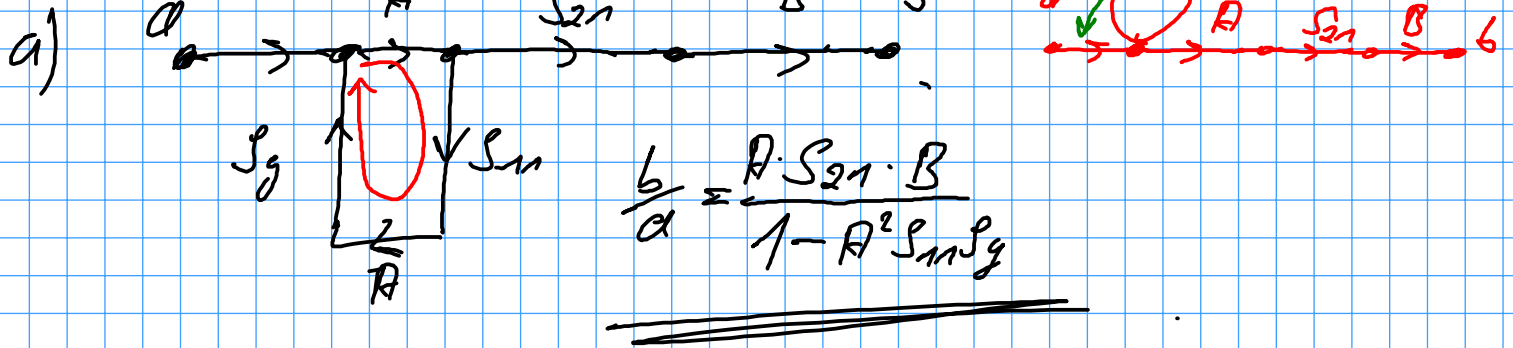

$$\frac{b}{a} = \frac{A S_{21} B}{1 - B^2 S_{22} S_2 - A^2 S_3 S_{11} + A^2 S_3 S_{11} B^2 S_{22} S_2 - A^2 S_{21} S_{22} B^2 S_3 S_3}$$

c) $\frac{b}{a} = \frac{A \cdot S_{21} \cdot B}{1 - A^2 S_{11} S_3}$ Ergebnis von a

$$S_{21} = \frac{\frac{b}{a} (1 - A^2 S_{11} S_3)}{AB}$$

a) $S_3 = -0,316$ oder $+0,316$

$$S_{21} = \frac{\frac{b}{a}}{AB} \cdot (1 - 0,316) \quad \text{oder} \quad \frac{\frac{b}{a}}{AB} \cdot (1 + 0,316)$$

$$0,684 \cdot \frac{\frac{b}{a}}{AB} < |S_{21}| < 1,316 \cdot \frac{\frac{b}{a}}{AB}$$

Fehler ca. $\pm 30\%$ in der Messung, wenn man S_3 ignoriert

mit $S_3 = \pm 0,1$ ist der Fehler dann $\pm 10\%$